



**CHITTAGONG UNIVERSITY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRONICS & TELECOMMUNICATION ENGINEERING
CHITTAGONG-4349, BANGLADESH.**

Course No. EEE-182

Course Title: Basic Electrical Engineering Sessional

Experiment No. 11

**TO MEASURE THE CURRENT, VOLTAGE AND TOTAL POWER
CONSUMPTION AND TO DRAW THE VECTOR DIAGRAM OF RLC SERIES &
PARALLEL CIRCUITS.**

PRELAB WORK:

- Read this laboratory manual carefully before coming to the laboratory class, so that you know what is required.
- Try to follow the lecture notes of EEE 111.
- **DONOT** copy others blindly!!!
- **Submit your lab report before the roll call.**



OBJECTIVE:

The objectives of the experiment are –

1. To measure current.
2. To measure voltage.
3. To measure power consumption.
4. To draw the vector diagram of RLC series and RLC parallel Circuit.

APPARATUS:

1. Three Ammeters.
 2. Three Voltmeters.
 3. Resistance with different values.
 4. Inductances.
 5. Capacitors.
 6. AC Source.
-

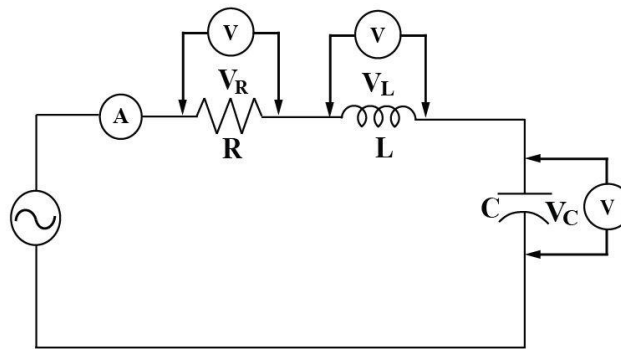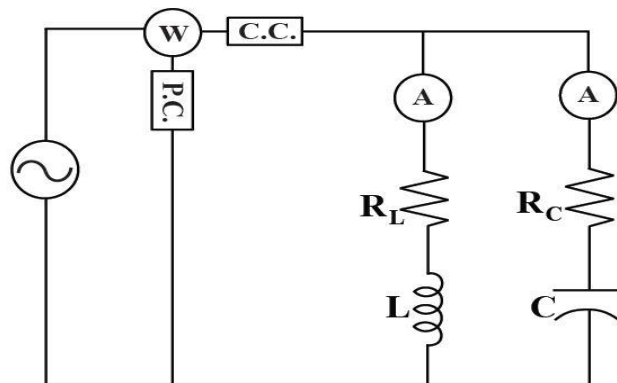CIRCUIT DIAGRAM:**Figure 1: RLC Series circuit.****Figure 2: RLC Parallel circuit.****PROCEDURE:****For RLC Series circuit**

1. Connect the circuit as shown above.
2. Take ammeter and voltmeter readings (I , V , V_R , V_L and V_C).
3. Take also wattmeter reading P .
4. Draw the vector diagram taking I as reference vector.
5. Find the power factor.

For RLC Parallel circuit

1. Connect the circuit as shown above.
2. Take meter readings of V , I_1 , I_2 and P . Also take the readings of V_{R1} , V_{R2} , V_C and V_L .
3. Draw the vector diagram taking as reference vector.
4. Find the power factor $\cos\theta$, $\cos\theta_1$, $\cos\theta_2$.
5. Calculate P_1 and P_2 .
- 6.

EXPERIMENTAL DATA:**For RLC Series circuit**

No. of obs.	I amps	V volts	V _R volts	V _L volts	V _C volts	cos θ	P watts

For RLC Parallel circuit

Nos of Obs	V _{R1} volts	V _L volts	V _{R2} volts	V _C volts	V volts	I ₁ amps	I ₂ amps	I amps	cos θ_1	cos θ_2	cos θ	P ₁ watts	P ₂ watts	P watts

REPORT:

1. Measure the current, voltage and power in RLC series and parallel circuits.
2. Also measure the power factor for two circuits.
3. Draw the vector diagrams for series and parallel circuit.

CAUTION:

1. Do not switch on the supply until the circuit has been checked by your teacher.
2. Take care of the apparatus.
3. Do not touch any open ended wire or cable with applying voltage supply at the other end.