



**CHITTAGONG UNIVERSITY OF ENGINEERING AND TECHNOLOGY  
DEPARTMENT OF ELECTRONICS & TELECOMMUNICATION ENGINEERING  
CHITTAGONG-4349, BANGLADESH.**

**Course No. EEE-182**

**Course Title: Basic Electrical Engineering Sessional**

**Experiment No. 5**

**VERIFICATION OF RECIPROCITY THEOREM AND COMPENSATION THEOREM**

**PRELAB WORK:**

- Read this laboratory manual carefully before coming to the laboratory class, so that you know what is required.
- Try to follow the lecture notes of EEE 111.
- **DONOT** copy others blindly!!!
- Submit your lab report before the roll call.

**(FOR RECIPROCITY THEOREM)**

**THEORY:**

In any linear bilateral network, if a source of emf  $E$  in any branch produces a current  $I$  in any other branch, then the same emf  $E$  acting in the second branch would produce the same current  $I$  in the first branch.

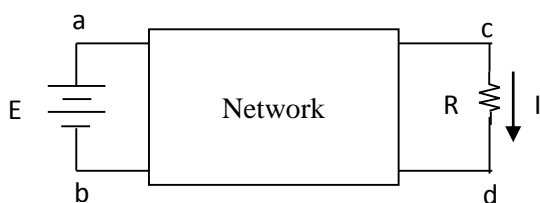


Figure-1

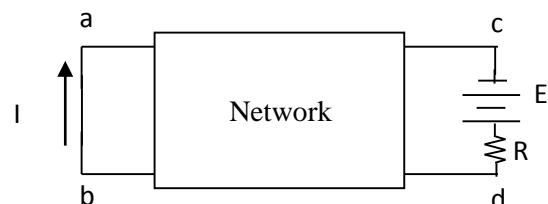


Figure-2

**APPARATUS:**

1. Resistors 120 $\Omega$ , 0.5 w (3 Pieces), 220  $\Omega$ , 0. 5w (2 pieces).
2. 470  $\Omega$ , 0. 25w (1 piece), 1K $\Omega$ , 0.25w (1 piece).
3. DC voltmeter.
4. DC ammeter.
5. Multimeter.
6. Bread Board.

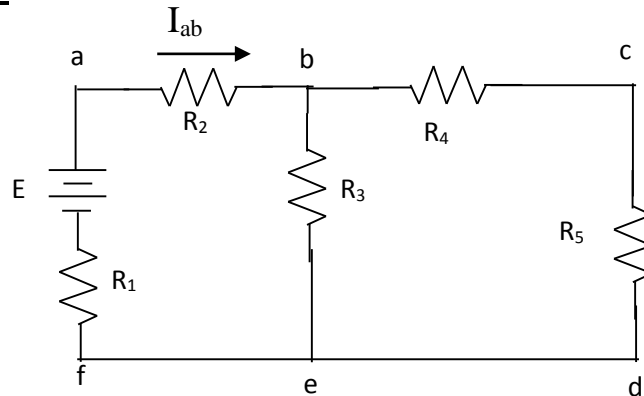
**CIRCUIT DIAGRAM:**

Figure-3

**PROCEDURES:**

1. Construct the circuit as shown in Fig. 3 with  $E=15\text{ Volts}$ ,  $R_1=120\ \Omega$ ,  $R_2=220\ \Omega$ ,  $R_3=120\ \Omega$ ,  $R_4=120\ \Omega$ ,  $R_5=220\ \Omega$ .
2. Now measure the currents in all branches and note down them in the Table-1.

**Table-1:**

When the source E is located in the branch 'af'

| $I_{ab}$ | $I_{be}$ | $I_{bc}$ | $I_{cd}$ |
|----------|----------|----------|----------|
|          |          |          |          |

3. Now replace the source of the 'af' branch with a short. Place the source E in the 'ab' branch with correct polarity so that the direction of current before and after the placement of the source is the same. Measure the current in 'fa' branch,  $I_{fa}(ab)$ .  $I_{fa}(ab)$  = Current in 'fa' branch when source is located in 'ab' branch. Note down this value in Table -2.

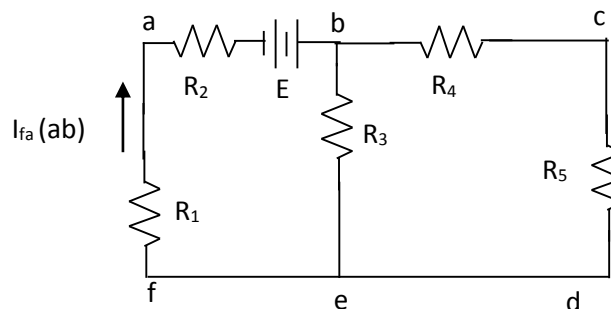


Figure-4

4. Similarly place the source in the branch 'be', 'bc', 'cd' step by step and measure the current in 'fa' branch at each step and put down these values in Table-2.

**Table-2:**

When the source E is located in different branch

| $I_{fa}(ab)$ | $I_{fa}(be)$ | $I_{fa}(bc)$ | $I_{fa}(cd)$ |
|--------------|--------------|--------------|--------------|
|              |              |              |              |

5. Now note down the actual values of  $E$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  &  $R_5$  for theoretical calculation.

### (FOR COMPENSATION THEOREM)

#### THEORY:

If the resistance of any branch of a network is changed from  $R$  to  $(R + \Delta R)$  where the current flowing originally is  $I$ , the change of current at any other place in the network may be found by assuming that an emf of  $-I \cdot \Delta R$  has been injected into the modified branch while all other sources are suppressed and are represented by internal resistances only.

#### CIRCUIT DIAGRAM

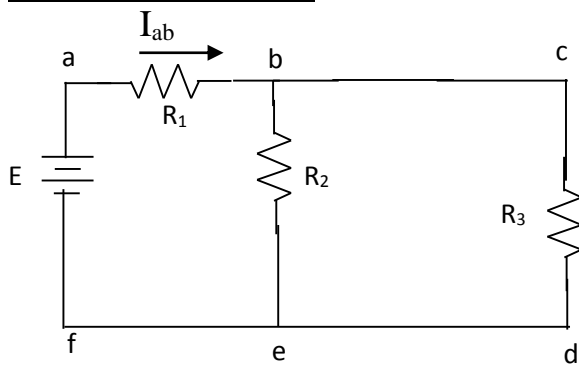


Figure-5

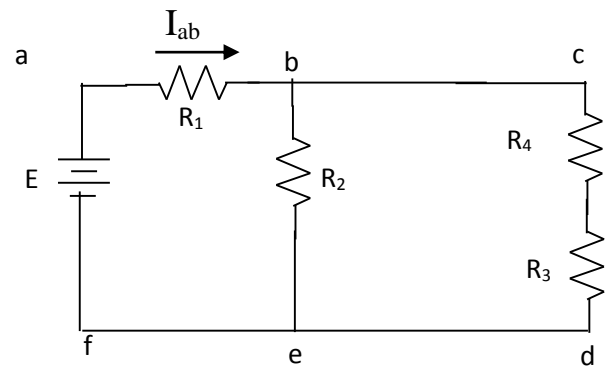


Figure-6

#### PROCEDURES:

1. Construct the circuit as shown in Fig. 5 with  $E=15$  Volts,  $R_1=220\ \Omega$ ,  $R_2=220\ \Omega$ ,  $R_3=470\ \Omega$ .
2. Now measure the currents in all branches and note down them in the Table-3.
3. Insert  $R_4=1000\ \Omega$  resistance in series with  $R_3=470\ \Omega$  in 'cd' branch as in Fig. 6 and again measure all branch currents and note down in Table-3.

Table-3:

|                                     | $I_{ab}$ | $I_{be}$ | $I_{cd}$ |
|-------------------------------------|----------|----------|----------|
| When $R_{cd}=470\ \Omega$           |          |          |          |
| When $R_{cd}=1470\ \Omega$          |          |          |          |
| Difference ( $I_{1470} - I_{470}$ ) |          |          |          |

4. Calculate the voltage,  $\Delta V = -I \times \Delta R = -I \times R_4$
5. Now apply a source of  $\Delta V$  volts in the 'cd' branch with correct polarity deactivating source  $E$  and measure the current in all branches and note down them in Table-4.

**Table-4:**

When the source  $\Delta V$  is located in the branch 'cd '

| $I_{ab}$ | $I_{be}$ | $I_{cd}$ |
|----------|----------|----------|
|          |          |          |

6. Now note down the actual values of  $E$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , &  $R_4$  for theoretical calculation

**REPORT:**

1. Verify the experimental results with those obtained by theoretical calculations.
2. Mention the applications of these theorems.