

# BJT

## Background

Vacuum tube:

- Expensive
- Large
- Power consumed
- Vacuum leaks
- Repeated heating

By  
MD TOUKIR SHAH  
EEE'18, CUET

## Moore's Law

Moore's law is the observation that the number of transistors in a dense integrated circuit (IC) doubles about every two years.

It is an observation and projection of a historical trend. Rather than a law of physics, it is an empirical relationship linked to gains from experience in production.

## Structure

- Three regions two pn junctions.
- Regions: Emitter, Base and collector
- Two types: npn and pnp
- Base in middle, emitter and collector are made of same semiconductor.
- Base  $\rightarrow$  Lightly doped and very thin.
- Emitter  $\rightarrow$  Heavily doped
- Collector  $\rightarrow$  Moderately doped.
- Total width to that of the center layer ratio 150:1.
- Doping of sandwiched layer to outer layer 10:1 or less.
- Bipolar: Both electron and hole conduct current/carriers.

## Operation (Amplifier)

- BE junction forward-Biased and BC junction Reverse-Biased.

→ Heavily doped n-type emitter region → free electrons → diffuse through the forward biased BE junction → lightly doped p-type base region → Base has low density of holes → majority carriers → small percentage of electron recombine with holes → move as valence electron → base region and into the emitter region as hole current.

→ Electrons recombined with holes → leave the crystalline structure → become free electron in the metallic base lead and produce the external base current.

→ Most of the electrons don't recombine with hole (base thin) → swept across into the collector region → positive collector supply → move through collector external circuit and return emitter region with base current.

$$I_E = I_B + I_C$$

$$1. \beta_{DC} = \frac{I_C}{I_B}$$

$$I_E = I_B + I_C$$

$$2. \alpha_{DC} = \frac{I_C}{I_E}$$

## Region of Operation

**Saturation:** Both junctions are forward-biased.


**Active/Linear:** BE forward  
BC reverse

**Cutoff:** Both reverse

### Cutoff


Base lead open.

$I_B = 0 \rightarrow \text{cutoff}$

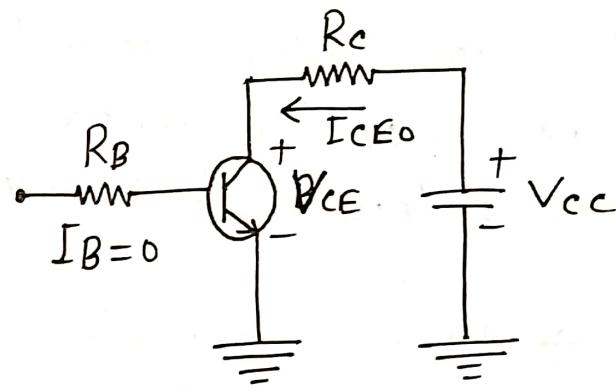

Small amount of collector leakage current,  $I_{CEO}$ .

## Saturation

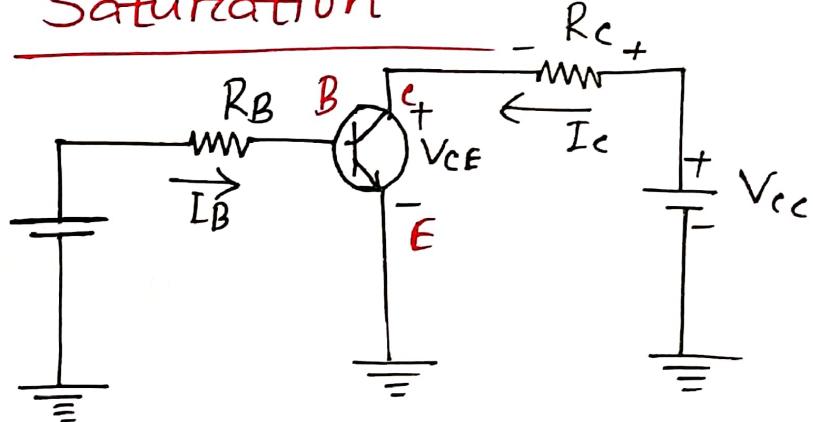

BE junction becomes forward  $\rightarrow I_B$  increases

$I_c$  also increases as  $I_c = \beta I_B$  and

$V_{CE}$  decreased as  $V_{CE} = V_{CC} - I_c R_C$


At saturation  $V_{CE}$  BC junction becomes forward biased,  $I_c$  can increase no further,  $I_c = \beta I_B$  not applicable.

DC Load Line

# Common Base

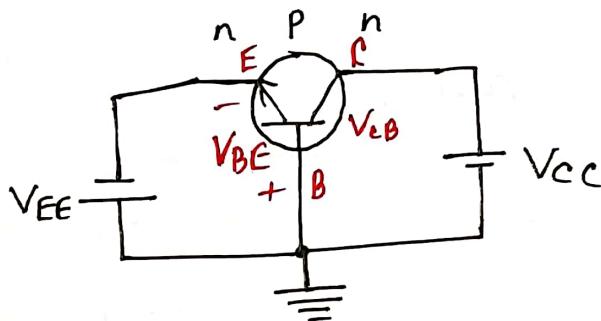
## Input characteristics : CB

- Base common
- Input: EB terminal and output: CB terminal.




- Same as the characteristics of Diode.

Input: IE and  $V_{BE}$  ||  $V_{CB}$  constant

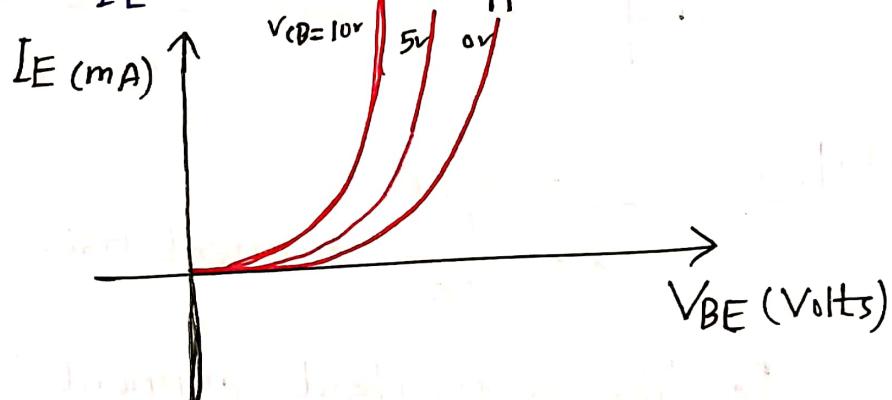

As the  $V_{CB}$  increases, the curve shifts left side,  $I_E$  also increases. As reverse bias increases, width of the depletion region also increases. Base narrow  $\rightarrow$  less voltage needed for forward biased.  $\therefore$  Curve shift.

Input impedance  $\rightarrow$  slope of the curve. (Very low)

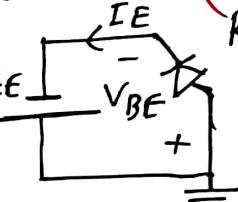Keeping  $V_{CB}$  at zero voltage: 

$$R_{in} = \frac{\Delta V_{BE}}{\Delta I_E}$$


$\uparrow$  small  
huge  
change  
 $\downarrow$   
Low

## Output characteristics of CB

Voltage:  $V_{CB}$

Current:  $I_C$

$$I_E = \text{constant}$$

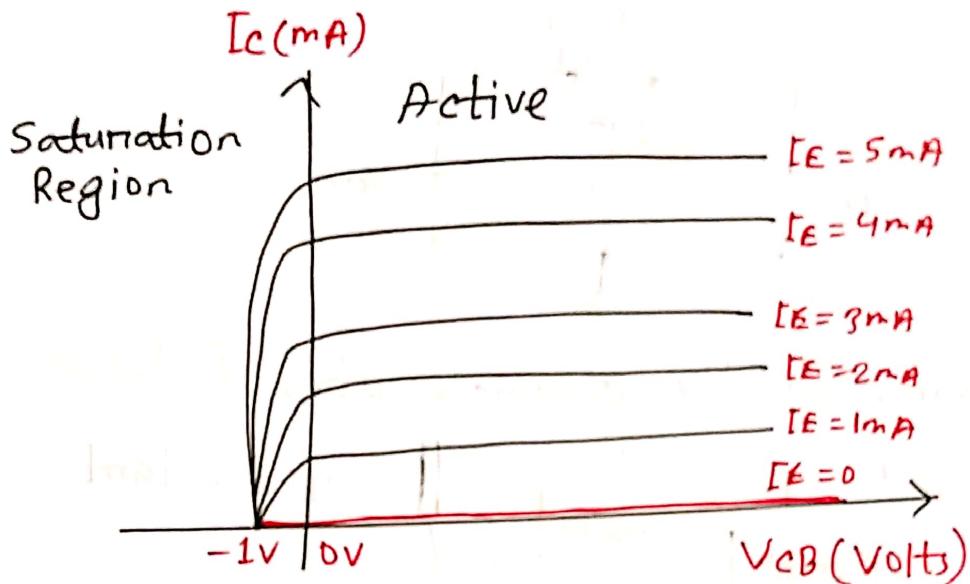

Active:  $I_C = \alpha I_E$

$$\alpha = \frac{\Gamma}{I_E} \text{ current gain}$$

$I_C$  like a constant current source.

For a fixed value of Emitter current,  $I_C$  is independent of  $V_{CB}$ . Region is used for Amplifiers as  $I_C$  only depends on input current  $I_E$ .

## Saturation:

$V_{CB}$  Reduced  $\rightarrow I_c$  starts reducing.

Reverse bias remove  $\rightarrow$  electron can not able to collector junction  $\rightarrow I_c$  reduced.

Both are forward  $\rightarrow$  saturation.

## Cutoff:

$I_E = 0 \rightarrow$  Even increases collector to Base voltage ( $V_{CB}$ )  $\rightarrow I_c = 0$

$V_{BE}$  removed  $\rightarrow I_E = 0$

$$I_c = \alpha I_E$$

$$\therefore I_c = 0$$

But small leakage current for minority carriers.

$$I_{cBO}$$

$$I_{cT} = I_c + I_{cBO}$$

$$I_{cT} = \alpha I_E + I_{cBO}$$


Output Impedance:  $R_o = \frac{\Delta V_{CB}}{\Delta I_c}$  High Low

Very High

## Common Base


### Input characteristics : C B

Forward Bias Diode.

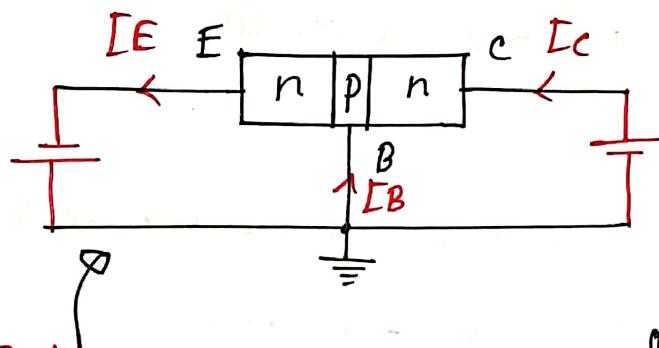

Active:


$i/p \ I = IE$	$\mid$	$\Phi/p \ I = I_c$
$i/p \ V = V_{BE}$	$\mid$	$\Phi/p \ V = V_{CB}$

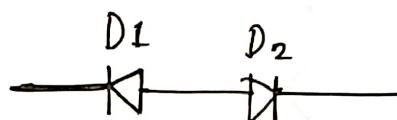

For active mode,


$D_1 \rightarrow$ Forward Bias
$D_2 \rightarrow$ Reverse Bias

$I_E(mA)$

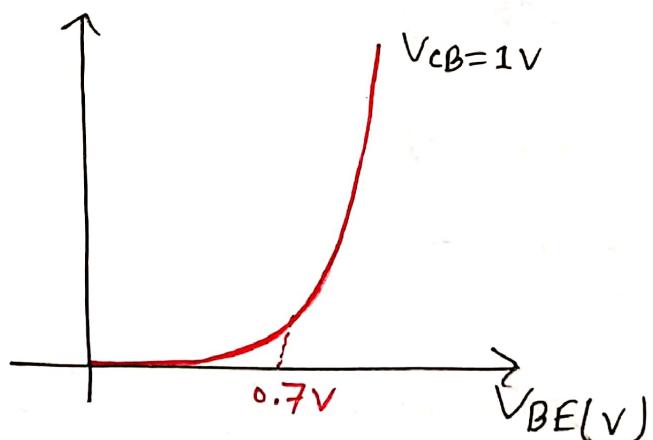

change  $V_{CB}$ : Early effect

## Early effect / Base width Modulation

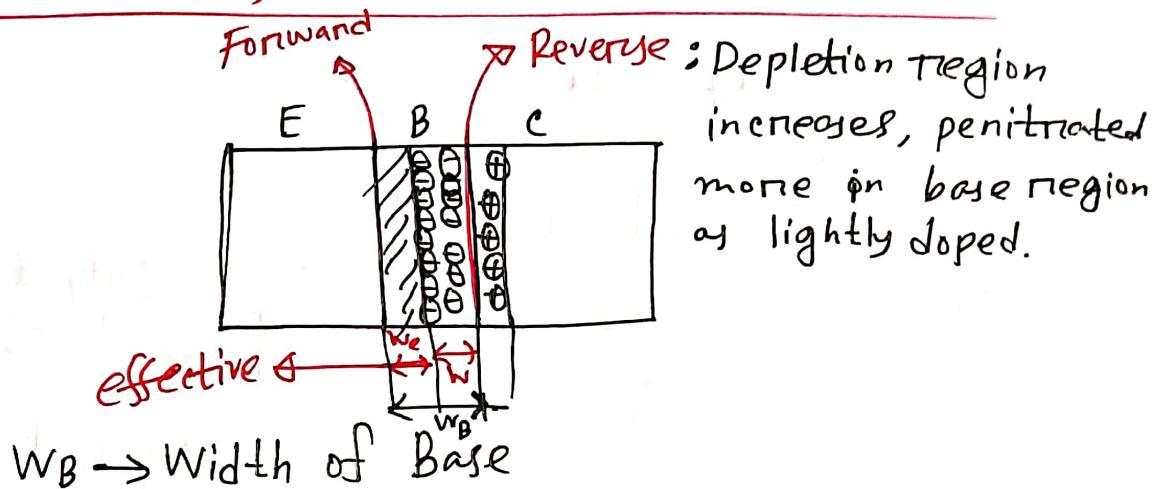

$$w_B = w_{eff} + w$$

$$w_{eff} = w_B - w$$


$$V_{CB} \uparrow \Rightarrow w \uparrow \Rightarrow w_{eff} \downarrow$$

Chance of recombination also decreases,


Input current  $I_E \uparrow$

Concentration Gradient: Increases

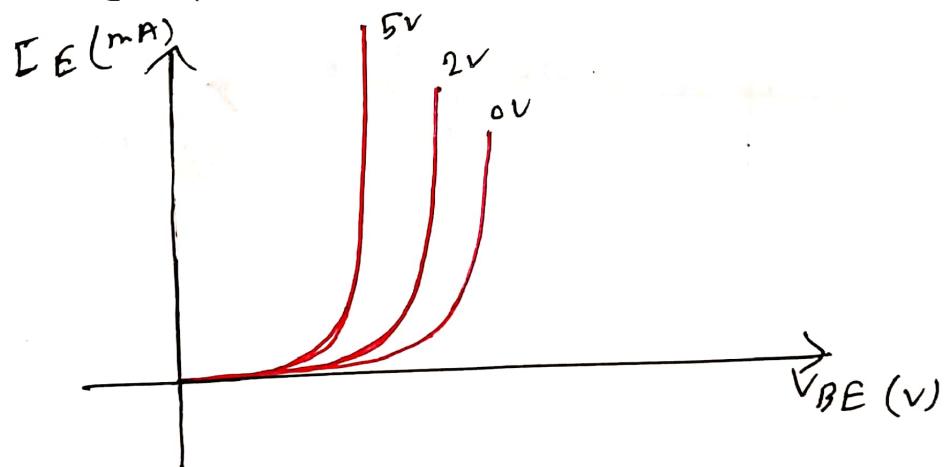
Electron movement increase  $\rightarrow I_E \uparrow$



## Output Characteristics of CB

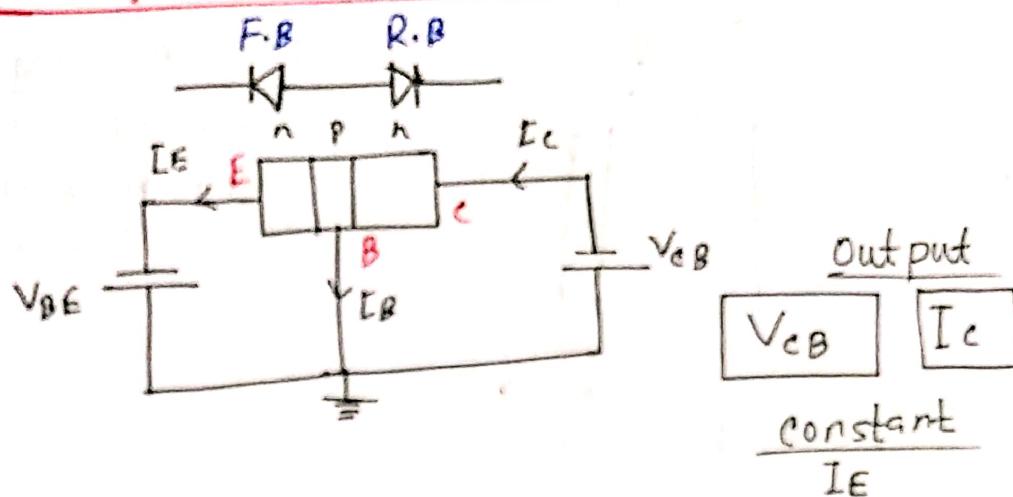


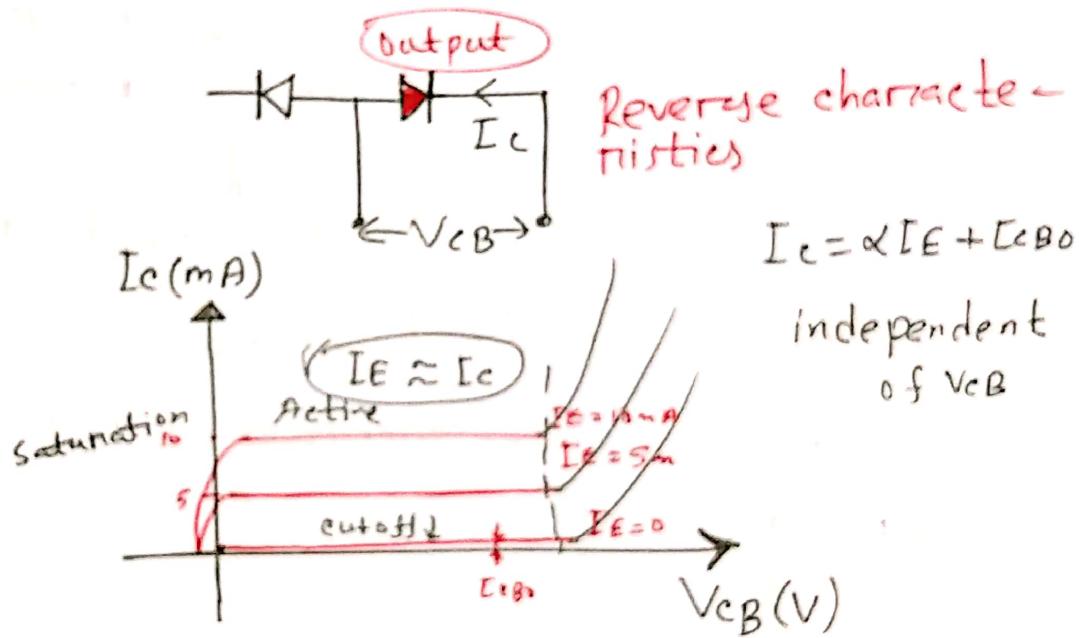Active: BE  $\rightarrow$  Forward }  $I_E \approx I_c$   
 CB  $\rightarrow$  Reverse }




## Common Emitter

Input characteristics: CE

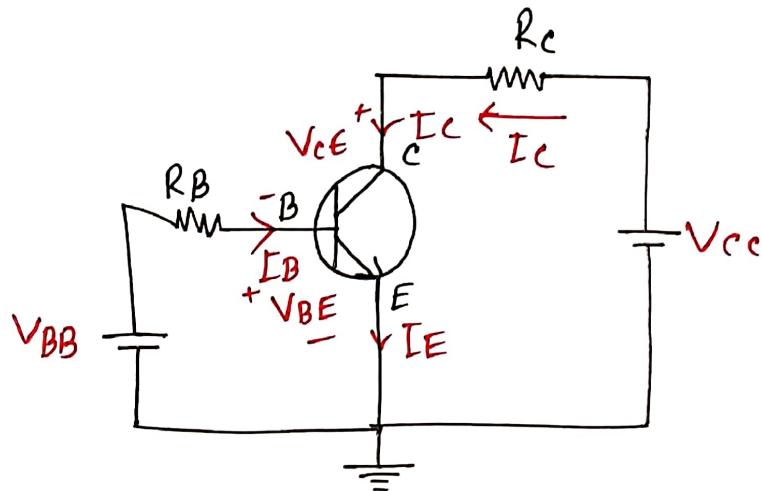

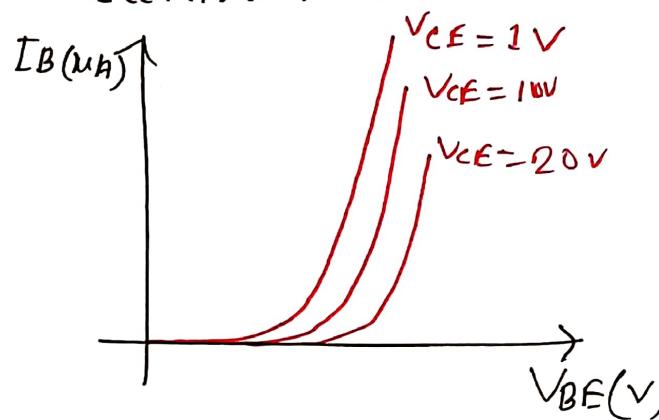The characteristics of the forward diode.




$V_{CE}$  increases Base current  $I_B$  reduces.

$$\uparrow V_{CE} = \uparrow V_{CB} + \boxed{V_{BE}} \text{ Fixed}$$

Reverse bias also increase in CB junction.


Recombination decreases.

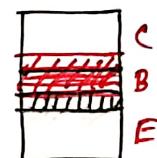Most of the electrons are collected by the collector terminal.



Output : CE

Output:  $I_C$  vs  $V_{CE}$

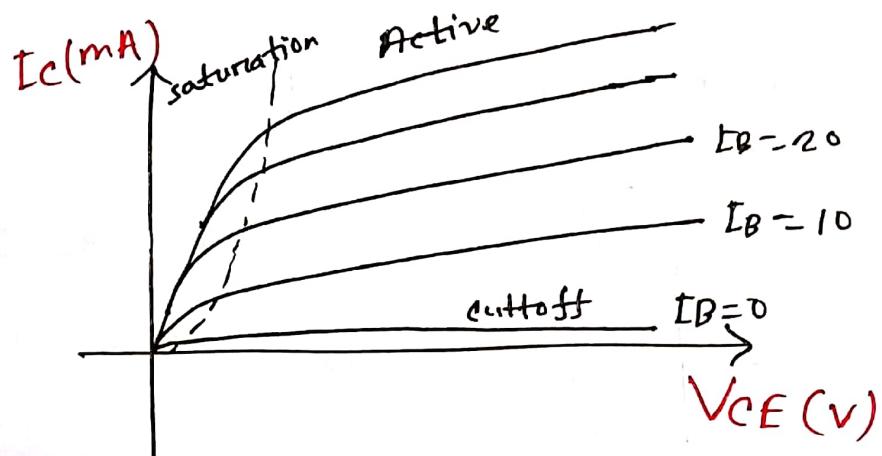

Active:  $I_B$  increases  $\rightarrow I_C$  increases

Not totally horizontal.

$V_{CE}$  increases  $\rightarrow V_{CB}$  also increases.

$$V_{CE} = V_{CB} + V_{BE}$$

$V_{CE}$  increases  $\rightarrow I_C$  also increase.

$$I_C = \beta I_B$$

Saturation:

CB forward Biased

cutoff

$$I_C = (\beta + 1) I_{CB0}$$

Leakage current

Cutoff:

$$I_B = 0$$

$I_C \rightarrow$  not zero (Large than CB)

$$I_B = 0$$

$$I_C = \alpha [E + I_{CB0}]$$

$$\Rightarrow I_C = \alpha (I_C + I_B) + I_{CB0}$$

$$\Rightarrow (1 - \alpha) I_C = \alpha I_B + I_{CB0}$$


$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CB0}$$

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CB0}$$

$$I_C = \frac{1}{1 - \alpha} I_{CB0} \quad (I_C \text{ high})$$


## Common Emitter

Input characteristics: CE

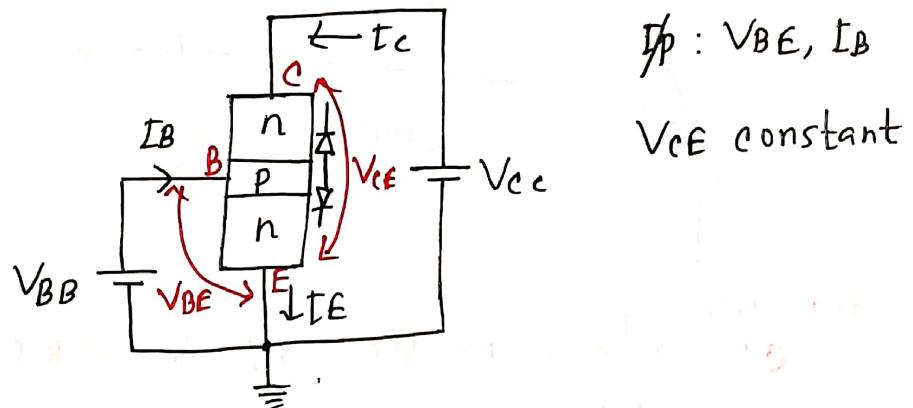


$\left\{ \begin{array}{l} \text{Current through the diode} \\ \text{Voltage across the diode} \end{array} \right.$

Characteristics of Diode

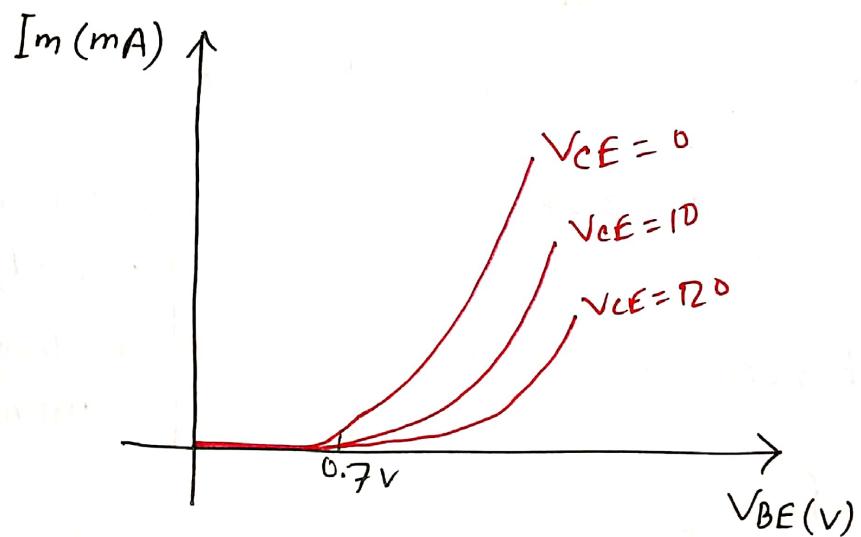

$V_{CE}$  effect: Early Effect

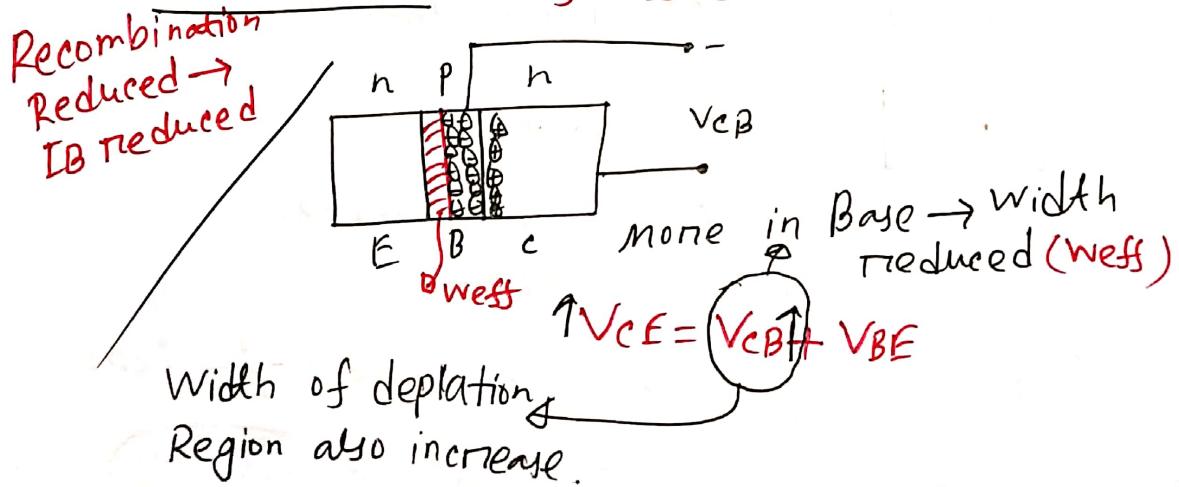


## Output characteristics: CE

O/P:  $I_C$  vs  $V_{CE}$  [ $I_B$  constant]

$$I_C = \beta I_B + (\beta + 1) I_{CBE}$$
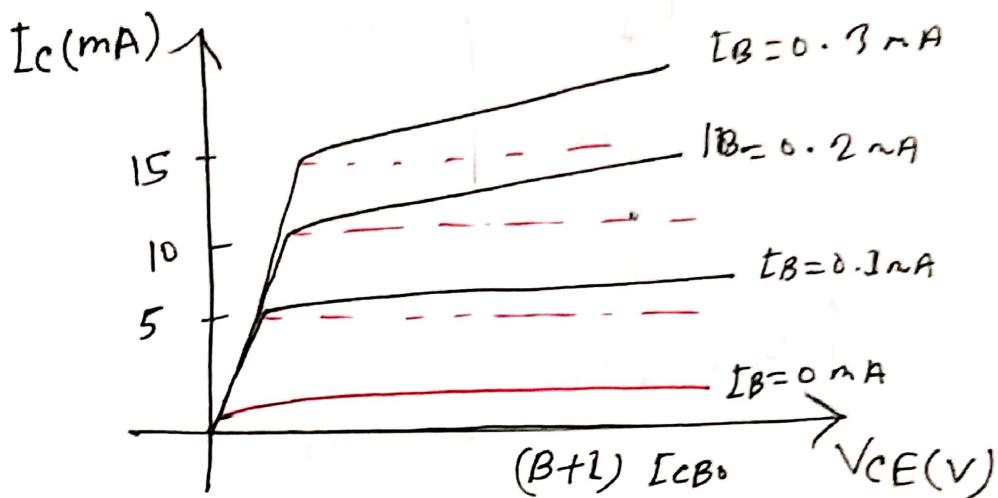
$$I_C = (\beta + 1) I_{CBO} \quad [I_B = 0]$$



$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad I_C \text{ depends } V_{CE}$$

$$\uparrow V_{CE} = \uparrow V_{CB} + V_{BE}$$

$W_{eff}$  decreases  $I_B$  decrease





$\nwarrow I_C$  current increases

#  $I_B$  depends on Both  $\begin{cases} \nearrow V_{CE} \\ \nearrow I_B \end{cases}$

# Common Collector

Input characteristics : CC

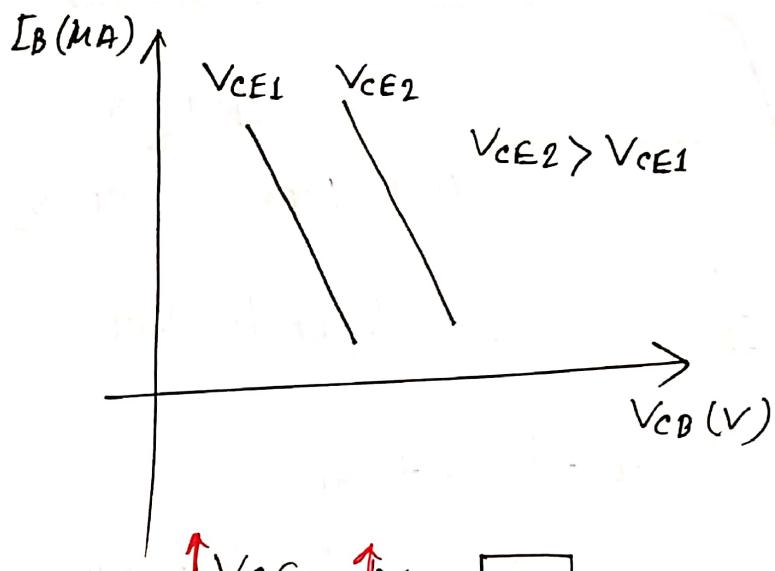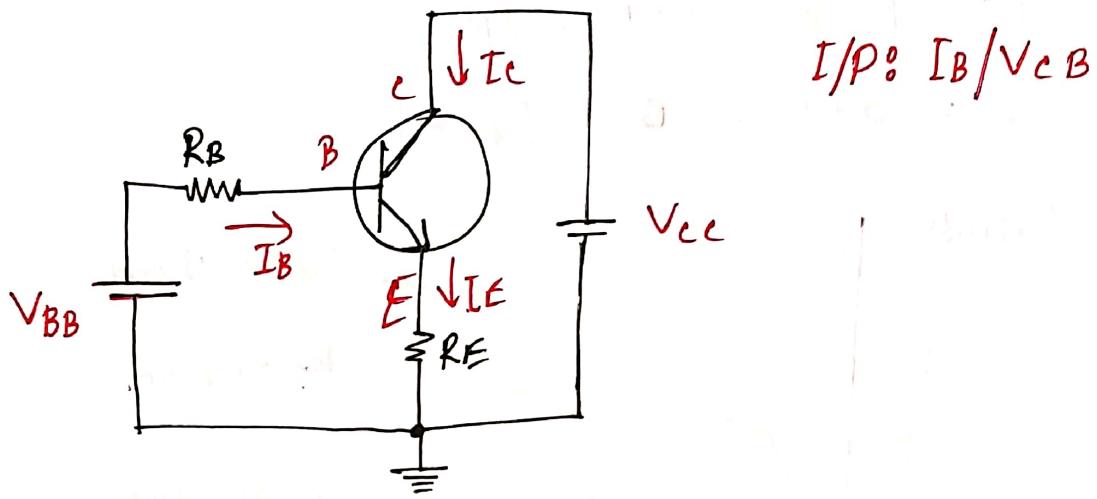

$$\uparrow V_{CE} = \uparrow V_{CB} + \boxed{V_{BE}}$$

$\left\{ \begin{array}{l} \text{Depletion Region Increases} \\ \text{Width decreases} \end{array} \right.$ 
  
Fixed

$I_B$  reduces

For  $V_{BE}$  increased  $\rightarrow$  More electrons pushed  $\rightarrow I_B$  increase.

$$\gamma = \frac{I_E}{I_B}$$

$$I_E = I_C + I_B$$

$$\gamma = \frac{I_C + I_B}{I_B} = \frac{I_C}{I_B} + 1$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\gamma = \beta + 1$$


$$\therefore \gamma = \frac{\alpha}{1-\alpha} + 1 = \frac{1}{1-\alpha}$$

$$\gamma = \beta + 1 = \frac{1}{1-\alpha}$$

$$\alpha \gamma = \frac{\alpha}{1-\alpha} = \beta$$

$$\alpha \gamma = \beta$$

**Output Characteristics: CC**

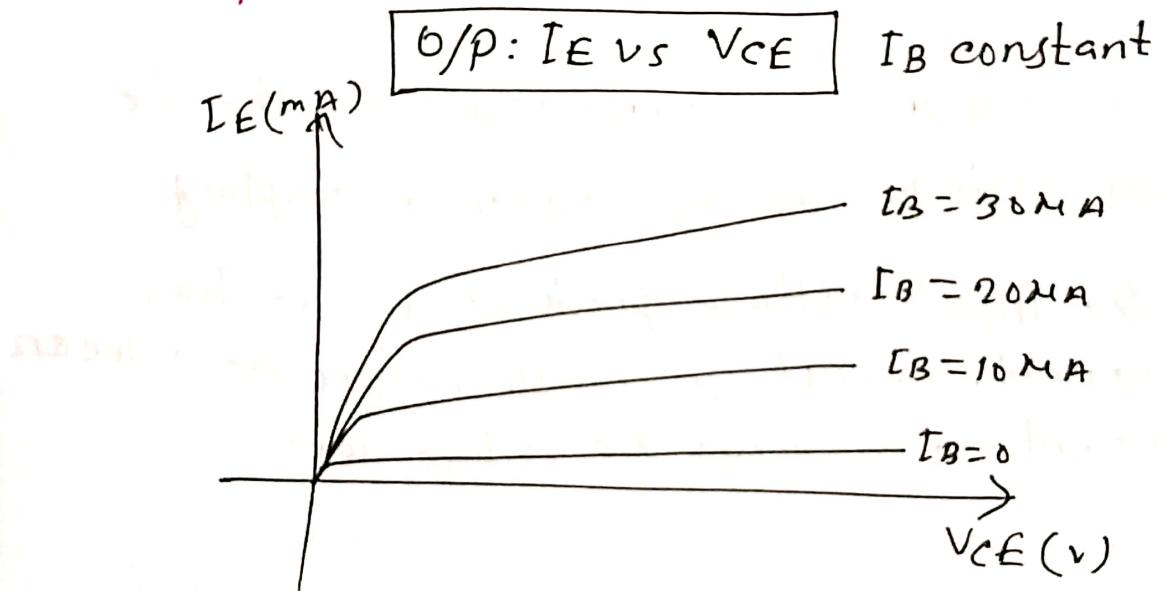


Same as CE configuration

$$I_E \approx I_C$$
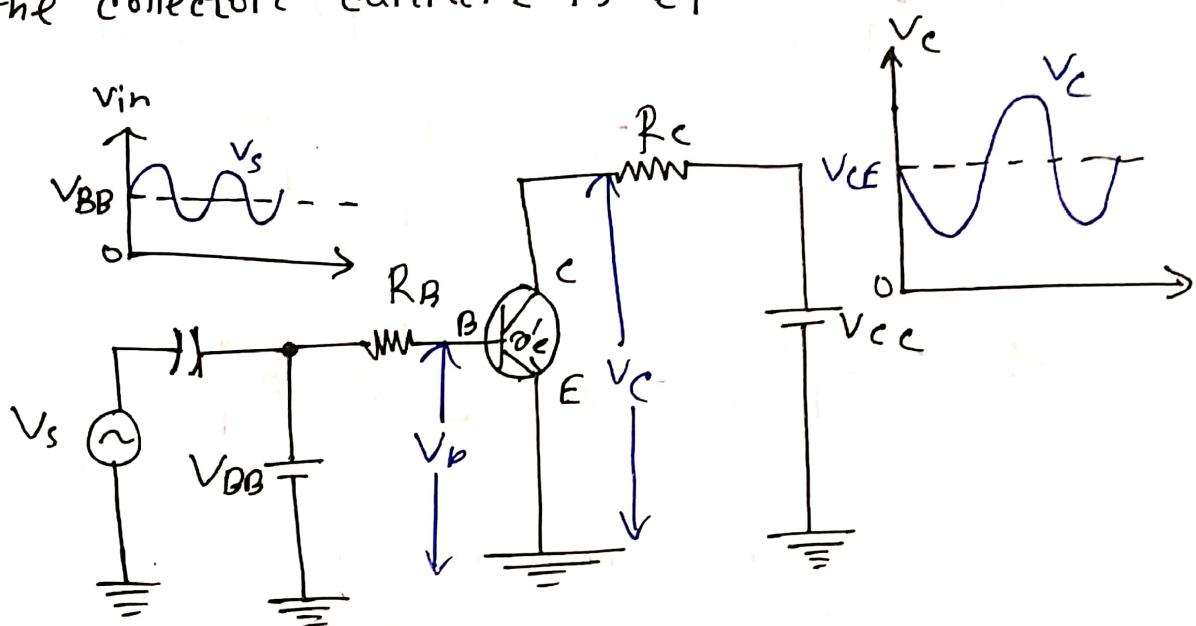
# BJT As An Amplifier

we know transistor amplifies current because the collector current is equal to  $B I_B$ .



- Ac voltage  $V_s$  superimposed on the dc bias voltage  $V_{BB}$  by capacitive coupling.
- Ac input voltage produces an ac base current, result in much larger ac collector current  $\rightarrow$  Produces Ac voltage across  $R_C$ .
- Thus produce an amplified, inverted, reproduction of the ac input voltage in the active region.
- $\rightarrow$  FB B-E junction presents a very low resistance ( $r_e'$ ), appear in series with  $R_B$ .

The ac base voltage:

$$V_b = I_e r_e$$

The ac collector voltage:

$$V_c = I_c R_c = I_e R_c \quad [\text{as } I_c \approx I_e]$$

Again,

$$V_b = V_s - I_b R_b = V_{in}$$

$$\text{Voltage gain, } A_v = \frac{V_c}{V_b} = \frac{I_e R_c}{I_e r_e}$$

$$\therefore A_v = \frac{R_c}{r_e}$$

Hence  $R_c$  is always larger than  $r_e$ .

# BJT as Switch

## Cutoff Region: OFF

Base-emitter junction is not forward biased, ideally open between collector and emitter. Can be indicated by switch equivalent.

Neglecting leakage current,  $V_{CE} = V_{CC}$ .

## Saturation: ON

BE and CB junctions both are forward biased.

Base current large enough to cause the collector current to reach its saturation value. In this condition there is a short (ideally) between collector and emitter.

$$I_c(sat) = \frac{V_{cc} - V_{CE(sat)}}{R_C} \xrightarrow{\text{can be neglected}}$$

Minimum Base current for saturation:

$$I_B(\min) = \frac{I_c(sat)}{\beta_{DC}}$$