

# Experiment 3

## Observation of Transistor Amplifier Circuits

Turja Roy  
2108052

January 28, 2024

### 1 Objective

1. To determine voltage, current, and power gain of common emitter amplifier configuration.
2. To determine voltage, current, and power gain of common base amplifier configuration.
3. To determine voltage, current, and power gain of common collector amplifier configuration.


### 2 Apparatus

1. Transistor (2N3904 n-p-n)
2. Resistors (1.2 k $\Omega$ , 3.6 k $\Omega$ , 10 k $\Omega$ , 20 k $\Omega$ , 220  $\Omega$ , 2.2 k $\Omega$ , 3.9 k $\Omega$ , 3.3 k $\Omega$ , 36 k $\Omega$ , 1 k $\Omega$ )
3. Capacitors (0.1  $\mu$ F, 10  $\mu$ F, 47  $\mu$ F)
4. Function generator
5. DC power supply
6. Oscilloscope
7. Breadboard, Wires, Multimeter, etc.


### 3 Circuit Diagrams

Below are the circuit diagrams for the three amplifier configurations.

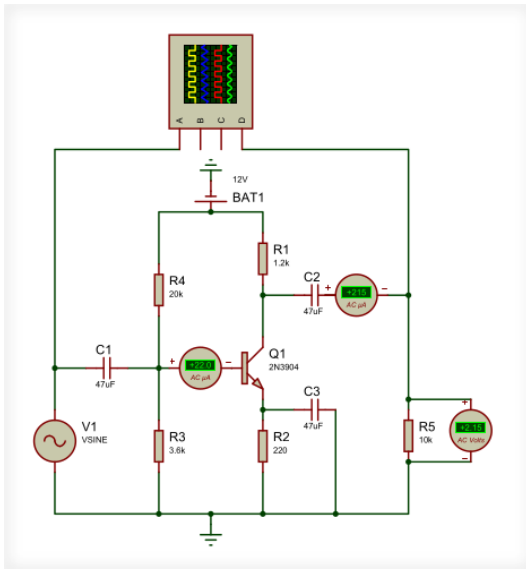
- (a) In common emitter amplifier, the input is applied between base and emitter, and the output is taken between collector and emitter. The emitter is common to both input and output.
- (b) In common base amplifier, the input is applied between base and emitter, and the output is taken between collector and base. The base is common to both input and output.
- (c) In common collector amplifier, the input is applied between base and emitter, and the output is taken between collector and base. The collector is common to both input and output.



(a) Common Emitter Amplifier

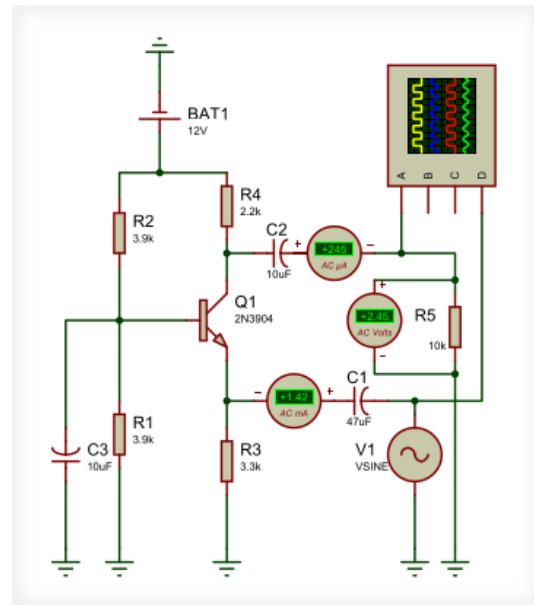

(b) Common Base Amplifier

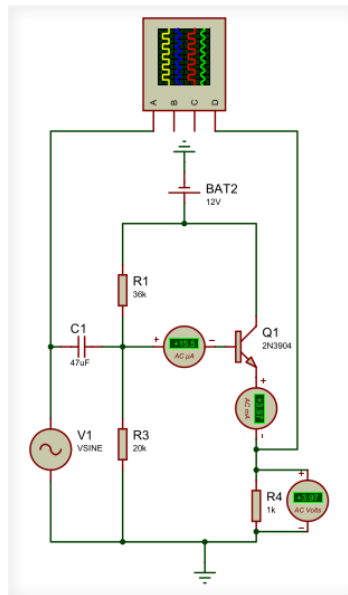

(c) Common Collector Amplifier

Figure 1: Amplifier Circuit Diagrams


## 4 Result Analysis

### 4.1 Common Emitter Amplifier


In common emitter amplifier, both voltage gain and current gain are obtained. The voltage gain is higher than the current gain. The amplified output is  $180^\circ$  phase shifted with respect to the input signal. Below are given the data table (Table 1), the simulated output signal (Figure 2(a)), and the practical output signal (Figure 2(b)).

Table 1: Data table for common emitter amplifier

Theoretical Data						
$V_{in}$ (mV)	$V_{out}$ (V)	$I_{in}$ ( $\mu$ A)	$I_{out}$ ( $\mu$ A)	$A_V$	$A_I$	$A_P$
100	2.244	22	222	22.44	10.09	226.44
Simulation Data						
$V_{in}$ (mV)	$V_{out}$ (V)	$I_{in}$ ( $\mu$ A)	$I_{out}$ ( $\mu$ A)	$A_V$	$A_I$	$A_P$
100	2.92	22	215	29.2	9.77	285.36
Practical Data						
$V_{in}$ (mV)	$V_{out}$ (V)	$I_{in}$ ( $\mu$ A)	$I_{out}$ ( $\mu$ A)	$A_V$	$A_I$	$A_P$
30	0.8	6.1	56.7	26.67	9.3	248.31

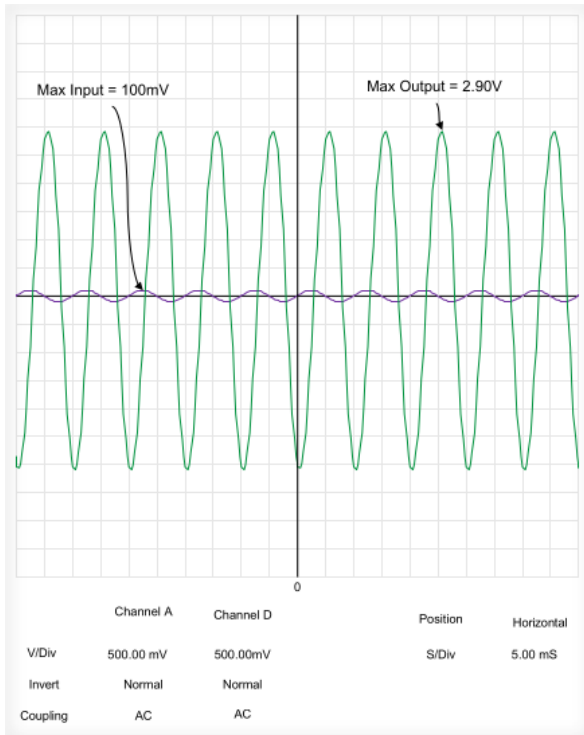

(a) Simulated output signal

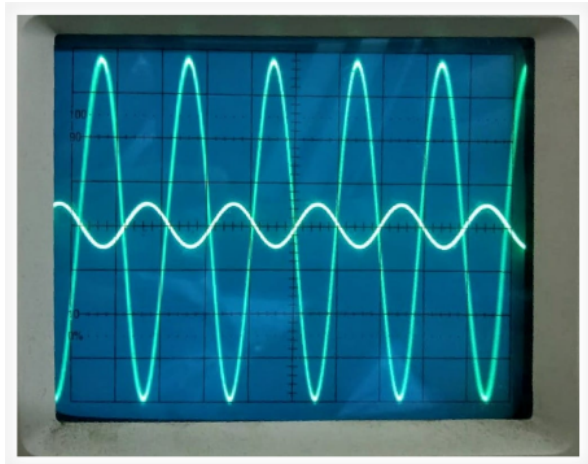

(b) Practical output signal


Figure 2: Common emitter amplifier output signal

## 4.2 Common Base Amplifier


In common base amplifier, the current gain is almost equal to 1. The voltage gain is almost same as the common emitter amplifier. Hence, the power gain of a common base amplifier is approximately equal to the voltage gain. Below are given the data table (Table 2), the simulated output signal (Figure 3(a)), and the practical output signal (Figure 3(b)).

Table 2: Data table for common base amplifier

Theoretical Data						
$V_{in}$ (mV)	$V_{out}$ (V)	$I_{in}$ (mA)	$I_{out}$ (mA)	$A_V$	$A_I$	$A_P$
100	11.204	6.19	6.13	112.04	0.99	110.95
Simulation Data						
$V_{in}$ (mV)	$V_{out}$ (V)	$I_{in}$ (mA)	$I_{out}$ (mA)	$A_V$	$A_I$	$A_P$
100	2.65	1.42	1.39	26.5	0.98	25.97
Practical Data						
$V_{in}$ (mV)	$V_{out}$ (V)	$I_{in}$ (mA)	$I_{out}$ (mA)	$A_V$	$A_I$	$A_P$
100	2.18	1.07	1.01	21.8	0.94	20.49

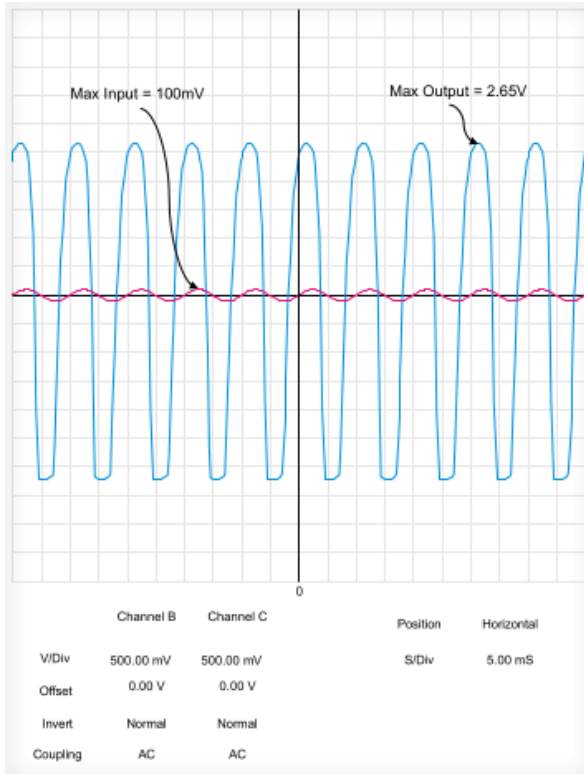

(a) Simulated output signal

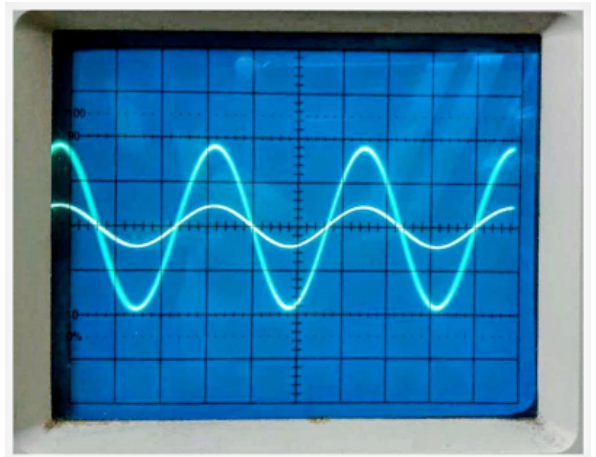

(b) Practical output signal


Figure 3: Common base amplifier output signal

### 4.3 Common Collector Amplifier


In common collector amplifier, the voltage gain is less than 1. The current gain is very high. Hence, the power gain of a common collector amplifier is approximately equal to the current gain. Below are given the data table (Table 3), the simulated output signal (Figure 4(a)), and the practical output signal (Figure 4(b)).

Table 3: Data table for common collector amplifier

Theoretical Data						
$V_{in}$ (V)	$V_{out}$ (V)	$I_{in}$ ( $\mu$ A)	$I_{out}$ (mA)	$A_V$	$A_I$	$A_P$
2.998	2.976	263.38	2.976	0.992	11.29	11.21
Simulation Data						
$V_{in}$ (V)	$V_{out}$ (V)	$I_{in}$ ( $\mu$ A)	$I_{out}$ (mA)	$A_V$	$A_I$	$A_P$
3	2.95	170	3.97	0.983	23.35	23.01
Practical Data						
$V_{in}$ (V)	$V_{out}$ (V)	$I_{in}$ ( $\mu$ A)	$I_{out}$ (mA)	$A_V$	$A_I$	$A_P$
3	2.35	135.56	4.37	0.783	32.22	25.25

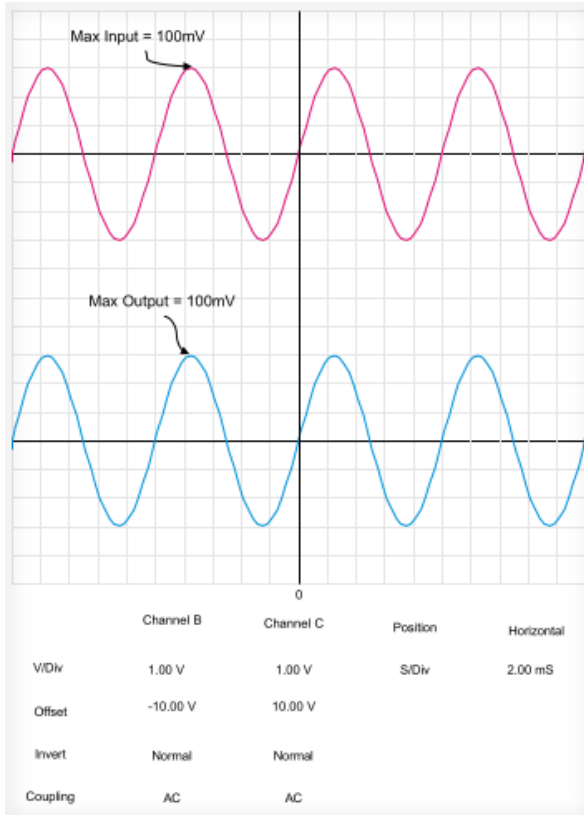

(a) Simulated output signal

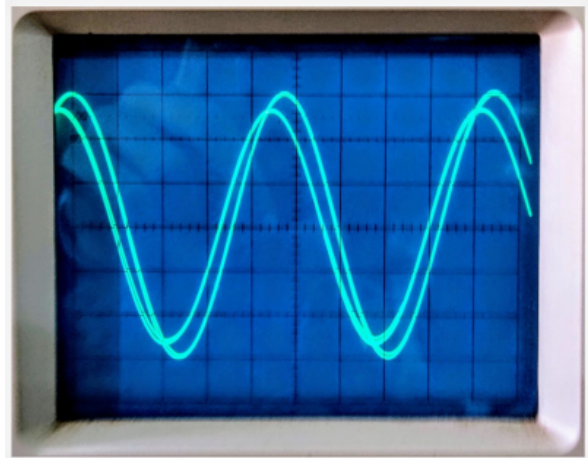

(b) Practical output signal

Figure 4: Common collector amplifier output signal

## 5 Discussion

From the experiment results, it can be seen that while the common emitter configuration has both voltage and current gain, the common base and common collector configurations have only voltage gain and current gain respectively. The current gain of common base is nearly 1 and the voltage gain of common collector is nearly 1. The common emitter configuration has the highest power gain among the three, followed by common collector and common base configurations respectively.

It was also observed that the output signal of common emitter amplifier is  $180^\circ$  phase shifted with respect to the input signal. The output signal of common base amplifier is in phase with the input signal. The output signal of common collector amplifier is slightly out of phase with respect to the input signal.

The discrepancies between the theoretical, simulated, and practical data can be attributed to different reasons. The theoretical data was calculated using ideal values, while the practical data was obtained using real components that have some tolerances. Temperature plays a role in BJT circuits since BJTs are more susceptible to thermal runaway. The errors could have been minimized by performing the experiment under a much more controlled environment.